

## Single-Phase Power Systems

In the United States 60Hz AC Electric power is typically supplied to a residence by a 240VAC center tapped transformer. This transformer may be supplied by one phase of a three-phase distribution system. It may be on a pole or underground. The transformer's center tap is connected to earth ground. Figure 3-5 is a simplified diagram showing a step-down transformer, power meter, and breaker panel.

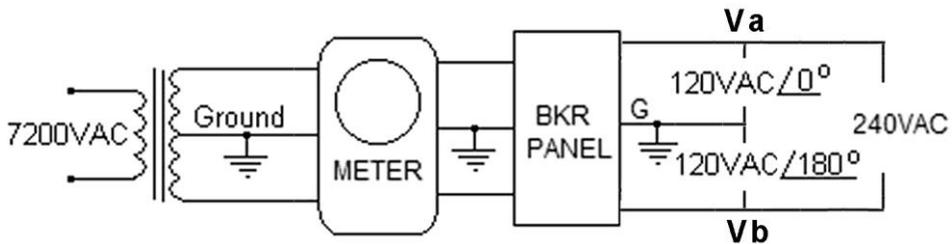


Figure 3-5

This transformer provides 120VAC on each side of the tap (**Va** to **G** and **Vb** to **G**) and 240VAC across the entire secondary (**Va** to **Vb**). Note that **Vb** to **G** is 180° out of phase with **Va** to **G**.

The actual voltage available at a 120VAC or 240VAC outlet is current dependent. The Voltage dropped across the transformer windings and distribution wires is proportional to current flow. This results in a power loss in the wiring resistance that is proportional to the square of the current. Other types of losses occur in power transformers which typically range from 2% to 4% of the power being supplied.

This chapter's Experiment 4 demonstrates some of the characteristics of a center tapped transformer distribution system. However, the voltages are scaled down so that the experiment may be safely performed on a breadboard. It uses the same transformer as used in Experiment 3.

The transformer is powered by a 400Hz sine wave from a signal generator. 400Hz is used here because the small 400mW transformer is less efficient at 60Hz. 400Hz is a common power distribution frequency on aircraft and marine vehicles because the transformers can be lighter. Alternately, a 12VAC center tapped line operated transformer could be used to do this experiment.

## Experiment 3b: Center Tapped Transformer

The operating characteristics of a center tapped transformer power source will be measured. The transformer's input power, output power, and efficiency will be determined.

### Equipment and Parts

Function Generator, Oscilloscope, DMM, and Breadboard.

Transformer, 500 $\Omega$  CT to 500 $\Omega$  CT, 400mW. Refer to appendix 2.

Recommended: ZICON 42TU500-RC (from Mouser Electronics)

Resistors: Two 10 $\Omega$ , three 470 $\Omega$ , all  $\frac{1}{4}$  watt, 5%.

### Procedure: Part 1, Balanced Load

1. Connect the circuit in Figure 3-6. Set the generator to produce a 400Hz, 12V p-p sine wave with no offset. Connect oscilloscope channel 1 to measure  $V_p$  and channel 2 to measure  $V_s$ . Trigger on channel 1.

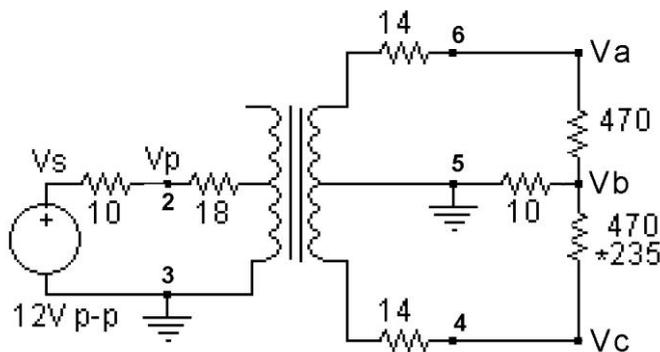


Figure 3-6

2. Measure and record the magnitude  $V_s$  and  $V_g$ .

$V_s$  \_\_\_\_\_ V p-p       $V_g$  \_\_\_\_\_ V p-p

3. Measure and record the magnitude and phase angle of the voltage  $V_a$  with channel 2 of the oscilloscope.

$V_a$ (mag.) \_\_\_\_\_ V p-p.       $V_a$ (angle) \_\_\_\_\_ degrees.

4. Measure and record the magnitude and phase angle of the voltage  $V_b$  with channel 2 of the oscilloscope.

$V_b(\text{mag.})$  \_\_\_\_\_ V p-p.       $V_b(\text{angle})$  \_\_\_\_\_ degrees.

5. Measure and record the magnitude and phase angle of the voltage  $V_c$  with channel 2 of the oscilloscope.

$V_c(\text{mag.})$  \_\_\_\_\_ V p-p.       $V_c(\text{angle})$  \_\_\_\_\_ degrees.

### Procedure: Part 2, Un-Balanced Load

1. Connect a 470 ohm resistor in parallel with the resistor connected between  $V_b$  and  $V_c$ .
2. Measure and record the magnitude  $V_s$  and  $V_g$ .

$V_s$  \_\_\_\_\_ V p-p       $V_g$  \_\_\_\_\_ V p-p

3. Measure and record the magnitude and phase angle of the voltage  $V_a$  with channel 2 of the oscilloscope.

$V_a(\text{mag.})$  \_\_\_\_\_ V p-p.       $V_a(\text{angle})$  \_\_\_\_\_ degrees.

4. Measure and record the magnitude and phase angle of the voltage  $V_b$  with channel 2 of the oscilloscope.

$V_b(\text{mag.})$  \_\_\_\_\_ V p-p.       $V_b(\text{angle})$  \_\_\_\_\_ degrees.

5. Measure and record the magnitude and phase angle of the voltage  $V_c$  with channel 2 of the oscilloscope.

$V_c(\text{mag.})$  \_\_\_\_\_ V p-p.       $V_c(\text{angle})$  \_\_\_\_\_ degrees.

Note: All of the voltage measurements in this experiment are in peak-to-peak units. Power must be calculated using RMS units. A spreadsheet may be used to convert the peak-to-peak units to RMS units and to calculate the transformer's power input and output.

## Analysis

1. Enter results into a spreadsheet. Calculate input power, output power and efficiency for parts 1 and 2. Refer to the example below:

	A	B	C	D	E	F	G	H	I	J	K
1	Part	Vs p-p	Vp p-p	Ip p-p	Va p-p	Vb p-p	Vc p-p	In p-p	Pin	Pout	%Eff.
2	1	12	11.57	0.043	10.43	0	10.43	0	0.062	0.058	93.05
4	2	12	11.4	0.06	9.95	0.188	8.69	0.019	0.086	0.061	71.85

Equations in cells: D2:  $=(B2-C2)/10$     H2:  $=F2/10$     I2:  $=(C2*D2)/8$   
 J2:  $=(E2+G2)^2/(8*940)$     K2:  $=(J2/I2)*100$

2. Explain the results for the phase angles between the source,  $V_p$ , and the voltages  $V_a$  and  $V_c$ .
3. Simulate the circuit of Figure 3-6 and compare your results to the to your measurements.
4. Calculate the output power for parts 1 and 2 using the ideal transformer model and compare the calculated results to your measurements and simulation.

## LTspice Example

The circuit in figure 3-7 below represents the circuit of part 2 of this experiment. It was simulated using the ideal transformer model and including the transformers primary and secondary resistances.

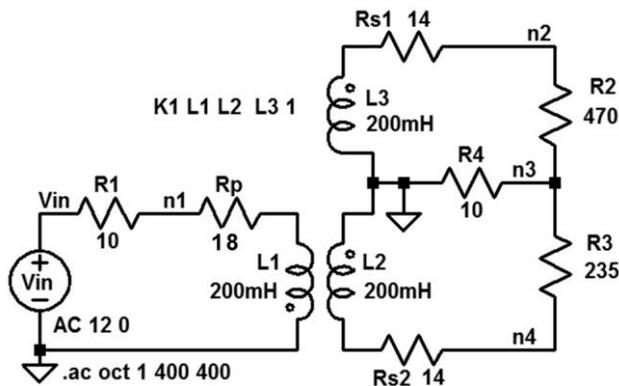


Figure 3-7

### Analysis Results

```

--- AC Analysis --- frequency:400Hz
V(vin): mag: 12.0    phase: 0.0°
V(n1):  mag: 11.37   phase: 0.8°
V(n2):  mag: 9.94    phase: -177.2°
V(n3):  mag: 0.18    phase: 2.7°
V(n4):  mag: 9.68    phase: 2.7°
    
```

In the circuit in figure 3-8 below the 10 ohm resistor between node n3 and ground is removed. It was simulated using the ideal transformer model and including the transformers primary and secondary resistances.

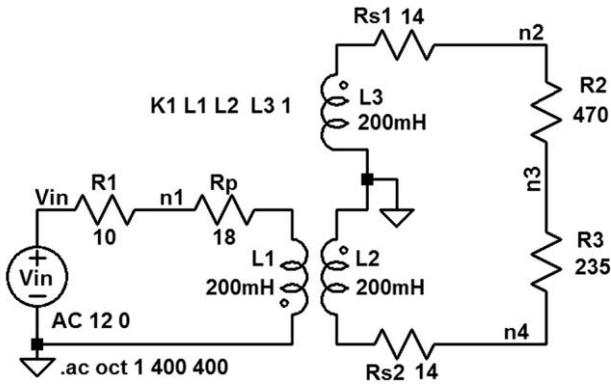


Figure 3-8

### Analysis Results

Note below that the voltage at node n3 is 3.33 volts. This causes the voltage across  $R2$  to increase to 13.33 volts and across  $R3$  to decrease to 6.67 volts.

```

frequency:400Hz --- AC Analysis ---
V(n1):  mag: 11.42   phase: 0.89°
V(vin): mag: 12.00   phase: 0.00°
V(n2):  mag: 10.00   phase: -177.23°
V(n3):  mag: 3.33    phase: 2.76°
V(n4):  mag: 10.00   phase: 2.76°
    
```