

## Experiment 5b: Delta-Wye transformer

A delta-wye configuration is typically used to step down transmission line and distribution line voltages. For example, it may be used to step down a 13.2KV distribution line voltage to a 240V/120V single-phase residential supply or a 208V/120V Three-phase commercial supply. A four wire service can provide Three phases of 208V line to line voltage and three phases of 120V line to neutral voltage.

### Equipment and Parts

Function Generator, Oscilloscope, DMM, and Breadboard.

Resistors: Three 10 $\Omega$ , three 1k, all  $\frac{1}{4}$  watt, 5%.

Capacitor: 0.68 $\mu$ F, 5%, Film type (4.7 $\mu$ F ceramic for 60Hz).

Transformer, Three 500 $\Omega$  CT to 500 $\Omega$  CT, 400mW (see appendix 2).

Recommended: ZICON 42TU500-RC (from Mouser Electronics)

Note: The specified 400mW transformer may be used at 60Hz. If 60Hz is used, use a 4.7 $\mu$ F capacitor instead of the 0.68 $\mu$ F. The results will show a somewhat lower efficiency.

### Procedure: Part 1, No Fault

1. Connect the circuit in Figure 5-5 below. **J1** is a jumper that will be connected for part 1 and part 3 of this experiment, and disconnected for part 2. The frequency of the Three-phase source is 400Hz. The amplitude of each phase is 12V p-p at the phase angles indicated.

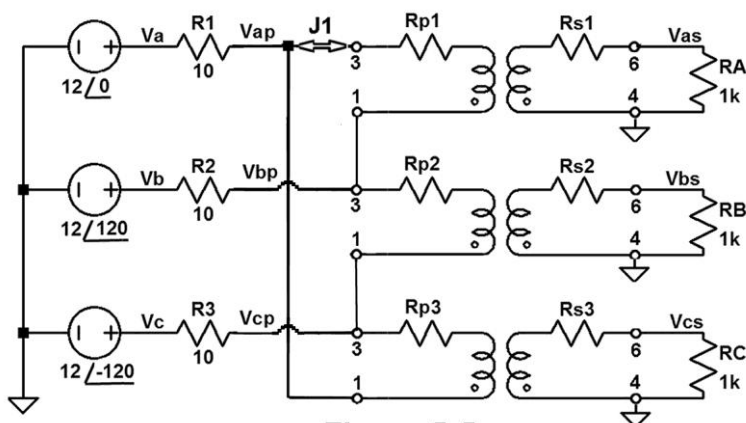


Figure 5-5

2. Connect oscilloscope channel 1 to **Va**. Trigger on channel 1. **Va** will be the reference phase for the entire experiment.
3. Measure and record the magnitude of **Va** and the magnitude and phase angle of **Vb**.

**Va:**\_\_\_\_\_ V p-p      **θa:** 0<sup>0</sup>      **Vb:**\_\_\_\_\_ V p-p      **θb:**\_\_\_\_\_<sup>0</sup>

Connect channel 2 of the oscilloscope to P2. Measure and record the magnitude of **Vc** and the magnitude and phase angle of **Vc**.

**Vc:**\_\_\_\_\_ V p-p      **θc:**\_\_\_\_\_<sup>0</sup>

4. Measure and record the primary voltages **Vap**, **Vbp**, and **Vcp**.

node		<b>Vap</b>	<b>Vbp</b>	<b>Vcp</b>
Mag. V p-p				
Angle Deg.				

5. Measure and record the secondary voltages **Vas**, **Vbs**, and **Vcs**.

node		<b>Vas</b>	<b>Vbs</b>	<b>Vcs</b>
Mag. V p-p				
Angle Deg.				

### Procedure: Part 2, Open Primary Winding

1. Remove the jumper **J1**.
2. Measure and record the primary voltages **Vap**, **Vbp**, and **Vcp**.

node		<b>Vap</b>	<b>Vbp</b>	<b>Vcp</b>
Mag. V p-p				
Angle Deg.				

3. Measure and record the secondary voltages **V<sub>as</sub>**, **V<sub>bs</sub>**, and **V<sub>cs</sub>**.

node		<b>V<sub>as</sub></b>	<b>V<sub>bs</sub></b>	<b>V<sub>cs</sub></b>
Mag. V p-p				
Angle Deg.				

### Procedure: Part 3, Reactive Load

1. Reconnect the jumper **J1**. Connect a 0.68 $\mu$ F capacitor across R<sub>c</sub> (4.7 $\mu$ F for 60Hz) .
2. Measure and record the primary voltages **V<sub>ap</sub>**, **V<sub>bp</sub>**, and **V<sub>cp</sub>**.

node		<b>V<sub>ap</sub></b>	<b>V<sub>bp</sub></b>	<b>V<sub>cp</sub></b>
Mag. V p-p				
Angle Deg.				

3. Measure and record the secondary voltages **V<sub>as</sub>**, **V<sub>bs</sub>**, and **V<sub>cs</sub>**.

node		<b>V<sub>as</sub></b>	<b>V<sub>bs</sub></b>	<b>V<sub>cs</sub></b>
Mag. V p-p				
Angle Deg.				

### Analysis, Part 1

Use the part 1 measurements to make the calculations below.

1. Calculate the primary currents, **I<sub>a</sub>**, **I<sub>b</sub>**, and **I<sub>c</sub>**.
2. Calculate the secondary line to line voltages and the total power, P, delivered to the load.
3. Calculate the total complex power, **S**, and total average power, P. Calculate the circuit's power factor.
4. Calculate the efficiency of the circuit and of the 3-phase transformer.
5. Compare your results to a simulation.

### Analysis, Part 2

Use the part 2 measurements to make the calculations below.

1. Calculate the primary currents, **I<sub>a</sub>**, **I<sub>b</sub>**, and **I<sub>c</sub>**.
2. Calculate the secondary line to line voltages and the total power, P, delivered to the load. Calculate the efficiency of the circuit.
3. Calculate the total complex power, **S**, and total average power, P. Calculate the circuit's power factor.
4. Explain the voltage across the load resistor, R<sub>a</sub>, when the primary winding of the phase **a** is open (R<sub>1</sub> removed).

### Analysis, Part 3

Use the part 3 measurements to make the calculations below.

1. Calculate the primary currents, **I<sub>a</sub>**, **I<sub>b</sub>**, and **I<sub>c</sub>**.
2. Calculate the secondary line to line voltages and the total power, P, delivered to the load.
3. Calculate the total complex power, **S**, and total average power, P. Calculate the circuit's power factor.
4. Compare your results to a simulation.

### LTspice Simulation

