

Using RC Filters as Phase Shifters

The Phase Tripler BD-3A60 from Antoch Labs uses a low-pass filter to obtain a -60 degree phase shift and a high-pass filter to obtain a +60 degree phase shift. Both filters are driven by the low output impedance of an op-amp so that the source resistance of V_{in} is close to zero ohms and can be neglected. Also, the output of both filters are connect to the very high input resistance of an op-amp so that the load resistance for V_o can be neglected. Refer to the diagrams and equations below.



LOW-PASS RC FILTER EQUATIONS.

$$V_o = \frac{-j \frac{1}{\omega C}}{R - j \frac{1}{\omega C}} = \frac{1}{1 + j\omega RC} V_{in}, \quad |V_o| = \frac{1}{\sqrt{1 + (\omega RC)^2}} |V_{in}|, \quad \theta = -\tan^{-1}(\omega RC), \quad RC = \frac{-\tan \theta}{\omega} = k,$$

$$C = \frac{k}{R}, \quad R = \frac{k}{C}. \quad \text{If } \theta = -60^\circ \text{ and } \omega = 377, \text{ then } k = 4.594 \times 10^{-3}. \quad \text{If } C = 56 \text{ nF}, R = 82 \text{ K}.$$

HIGH-PASS RC FILTER EQUATIONS.

$$V_o = \frac{R}{R + j \frac{1}{\omega C}} = \frac{1}{1 + j \frac{1}{\omega RC}} V_{in}, \quad |V_o| = \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}} |V_{in}|, \quad \theta = \tan^{-1}\left(\frac{1}{\omega RC}\right), \quad RC = \frac{1}{\omega \tan \theta} = k,$$

$$C = \frac{k}{R}, \quad R = \frac{k}{C}. \quad \text{If } \theta = -60^\circ \text{ and } \omega = 377, \text{ then } k = 1.531 \times 10^{-3}. \quad \text{If } C = 56 \text{ nF}, R = 27.35 \text{ K}.$$

The magnitude of the output is exactly one-half of the input voltage for both the low-pass and the high-pass filter.

$$\frac{|V_o|}{|V_{in}|} = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (377 \cdot 82000 \cdot 56 \times 10^{-9})^2}} = \frac{1}{2}$$

The values of R and C for each filter are chosen so that the filters present a reasonable load to the op-amp output and so that precision resistors and capacitors are available for the chosen R and C values. This usually requires choosing an available capacitor value and calculating the required resistor value. If the resistor value is not commercially available, choose another capacitor value and repeat the calculation.